

ECE 485/585

Computer Organization and Design

Lecture 6: ALU Design

Fall 2022

Won-Jae Yi, Ph.D.

Department of Electrical and Computer Engineering
Illinois Institute of Technology

Outline

- 1-Bit ALU Design
 - Logical operations
 - Addition
 - Subtraction
 - Conditional branch
- 32-Bit ALU Design
- Faster Adder Implementation


Logic Design Basics

- Information encoded in binary
 - Low voltage = 0, High voltage = 1
 - One wire per bit
 - Multi-bit data encoded on multi-wire buses
- Combinational element
 - Operate on data
 - Output is a function of input
- State (sequential) elements
 - Store information

Combinational Elements


- AND-gate

- $Y = A \& B$

 


- Adder

- $Y = A + B$

 


- Multiplexer

- $Y = S ? I1 : I0$

 



- Arithmetic/Logic Unit

- $Y = F(A, B)$

 



Sequential Elements

  - Register: stores data in a circuit
 - Uses a clock signal to determine when to update the stored value
 - Edge-triggered: update when Clk changes from 0 to 1





Sequential Elements

  - Register with write control
 - Only updates on clock edge when write control input is 1
 - Used when stored value is required later



Clocking Methodology

  - Combinational logic transforms data during clock cycles
 - Between clock edges
 - Input from state elements, output to state element
 - Longest delay determines clock period




Arithmetic Logic Unit (ALU)

- Datapath and Control unit are the main components of any processing unit
 - ALU is part of the datapath system
 - Computations are done in ALU
- ALU design using only AND, OR, inverter gates and multiplexors
- 32-bit ALU for MIPS
 - First build a 1-bit ALU
 - Use 32 1-bit ALUs to form 32-bit ALU

ALU Interface


- We will be designing a 32-bit ALU with the following interface:

ALU control lines	Function
0000	AND
0001	OR
0010	add
0110	subtract
0111	set on less than
1100	NOR

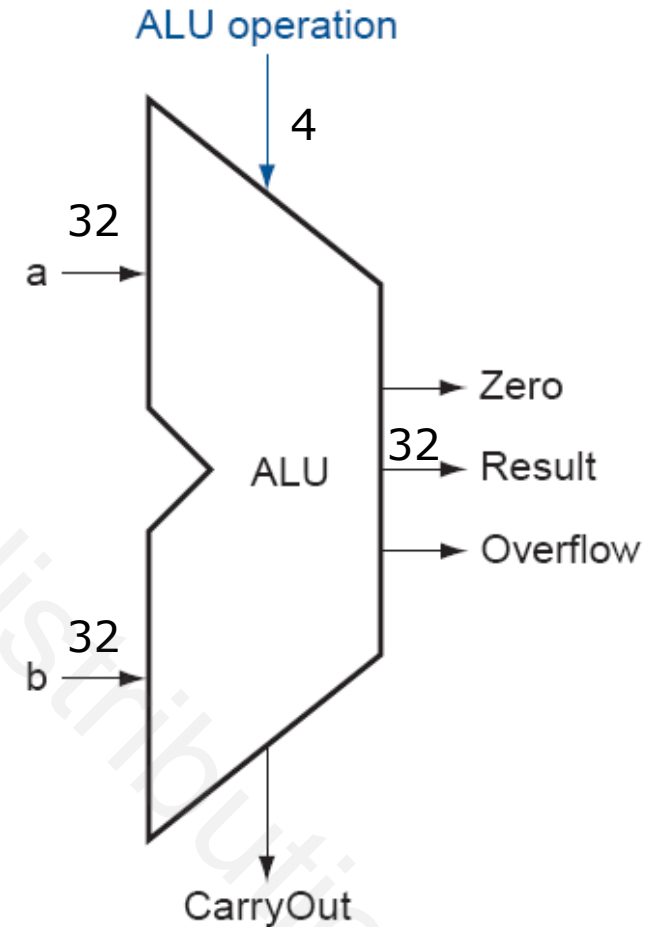

1-Bit ALU

 - Start with simple operations and build upon it
- Logical Operations for 1-Bit ALU:
 - AND
 - OR




1-bit logical unit for AND and OR

- The function of the ALU is determined by the control signals for the multiplexor

Addition

 - Full-Adder (3,2) adder:
 - Each adder has 3 inputs:
 - 2 inputs for the operands
 - 1 input for the *CarryIn*
 - Each adder has 2 outputs
 - 1 output for the result
 - 1 output for the *CarryOut*



- Half-Adder (2,2) adder
 - Each half-adder has 2 inputs (no *CarryIn*)

Full Adder


- Input/Output specifications for a 1-bit adder

Inputs			Outputs		Comments
a	b	CarryIn	CarryOut	Sum	
0	0	0	0	0	$0 + 0 + 0 = 00_{\text{two}}$
0	0	1	0	1	$0 + 0 + 1 = 01_{\text{two}}$
0	1	0	0	1	$0 + 1 + 0 = 01_{\text{two}}$
0	1	1	1	0	$0 + 1 + 1 = 10_{\text{two}}$
1	0	0	0	1	$1 + 0 + 0 = 01_{\text{two}}$
1	0	1	1	0	$1 + 0 + 1 = 10_{\text{two}}$
1	1	0	1	0	$1 + 1 + 0 = 10_{\text{two}}$
1	1	1	1	1	$1 + 1 + 1 = 11_{\text{two}}$

Full Adder


$$\text{CarryOut} = (b \cdot \text{CarryIn}) + (a \cdot \text{CarryIn}) + (a \cdot b)$$
 
$$\text{SUM} = (a \cdot \bar{b} \cdot \overline{\text{CarryIn}}) + (\bar{a} \cdot b \cdot \overline{\text{CarryIn}}) + (\bar{a} \cdot \bar{b} \cdot \text{CarryIn}) + (a \cdot b \cdot \text{CarryIn})$$




Expanding ALU Hardware

 - Add more functionality by expanding the multiplexor
 - Additional inputs and control lines



Subtraction

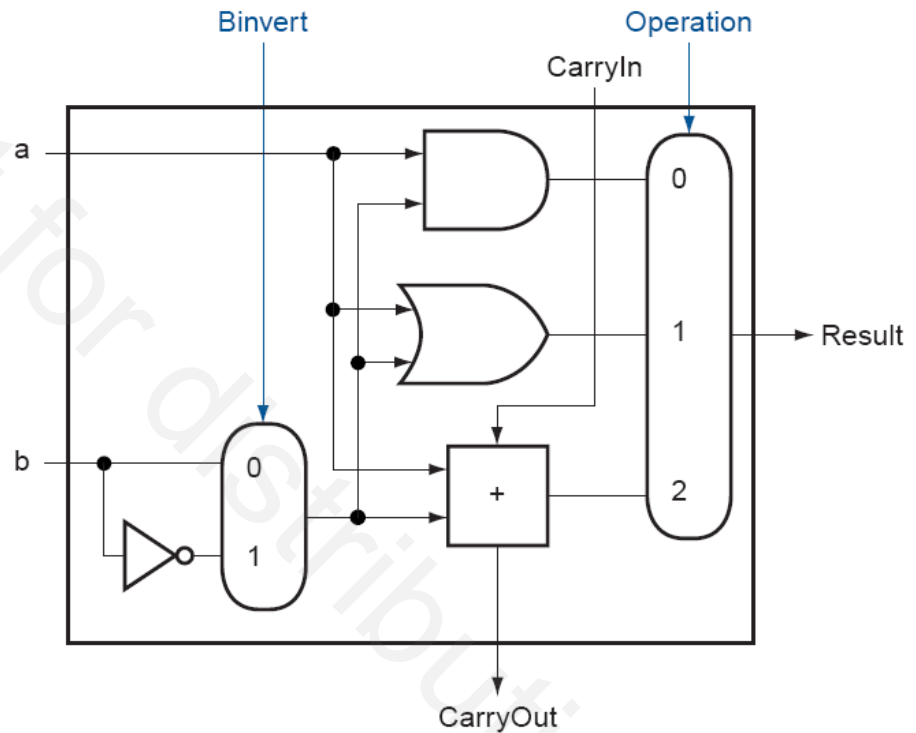- Subtraction is the same as adding the negative version of the operand
 - Invert each bit and add 1
- Add a new multiplexor to invert the operand **b**




NOR Gate

- Use the existing hardware in the ALU:

According to DeMorgan's:


$$\overline{(a + b)} = \overline{a} \cdot \overline{b}$$

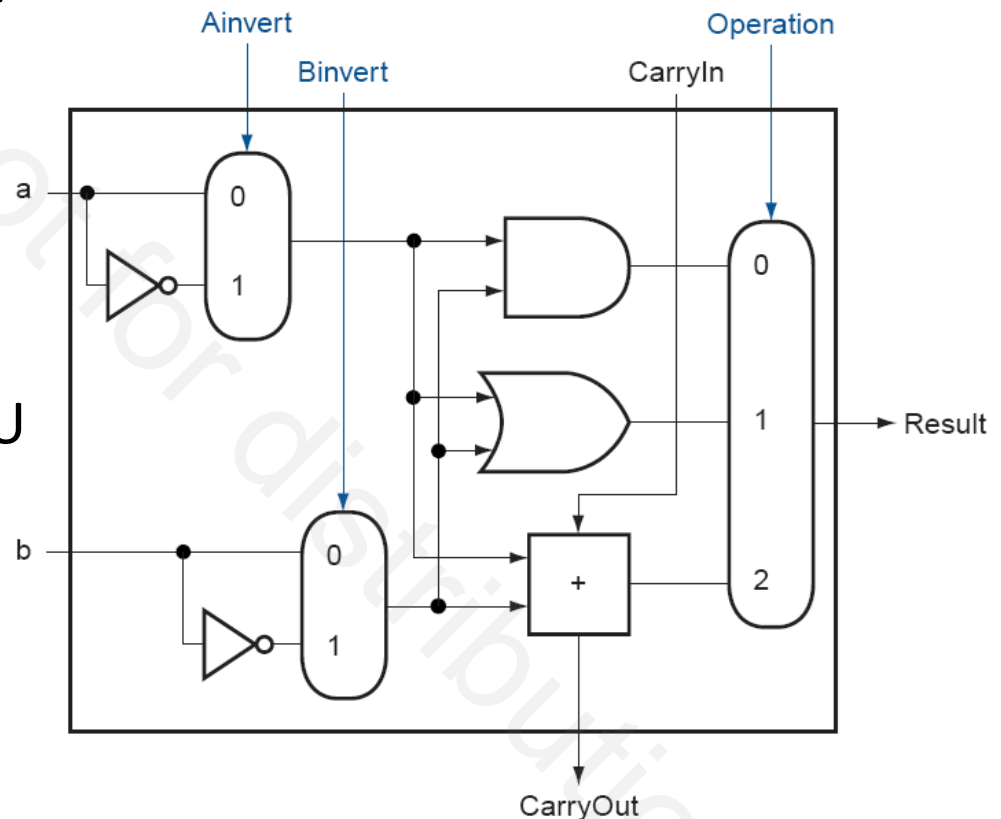- AND** gate and **NOT** **b** already exists;
 - add **NOT** **a** to the ALU
- Another Multiplexor and an inverter



32-bit ALU

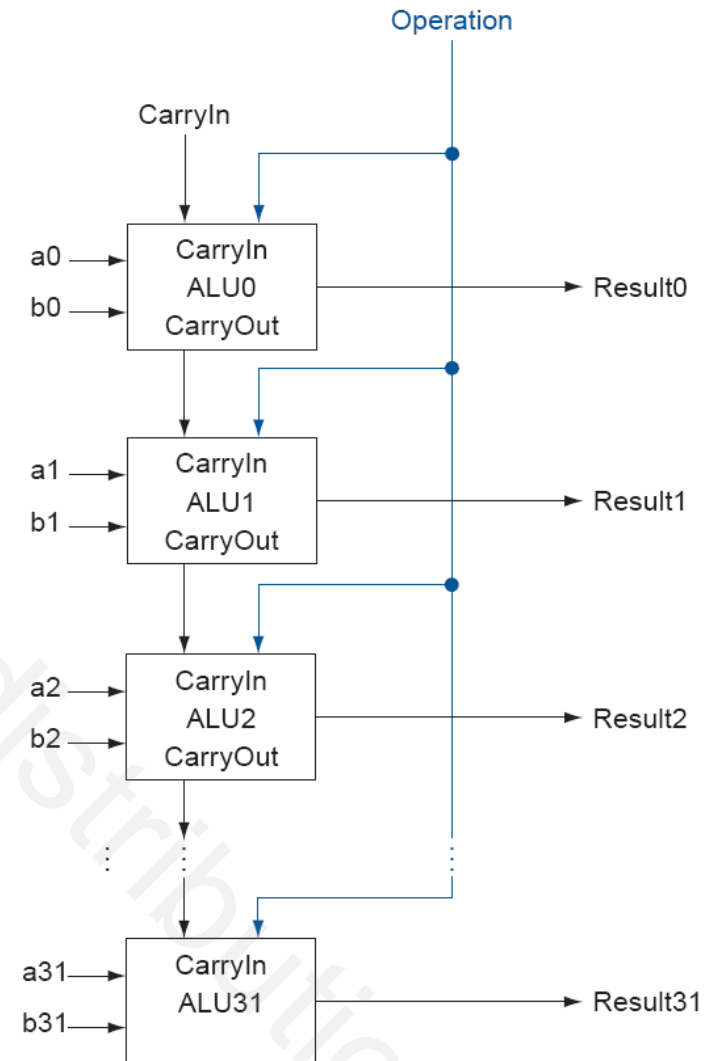- Full 32-bit ALU can be created by connecting the adjacent 1-bit ALU's
- Results will ripple from the least significant bit **Result0** to most significant bit **Result31**
- **Ripple-Carry** adder




Set-on-Less-Than (slt) Instruction

- **slt**: compares two registers $r_s < r_t$
 - If $r_s < r_t$ then r_d set to 1; else r_d clear to 0.
- Another input (**Less**) required for the Result multiplexor:
 - connect 0 to **Less** input of upper 31 bits;
 - What about the least significant bit?
- Subtract (**a-b**) and the sign bit will determine the value for less input for the least significant bit
- A new output bit **SET** (adder output) is required for the most significant bit in the ALU

1-bit ALU for the MSB

- Overflow logic can also be integrated into most significant ALU bit

$$V = C_n \otimes C_{n-1}$$

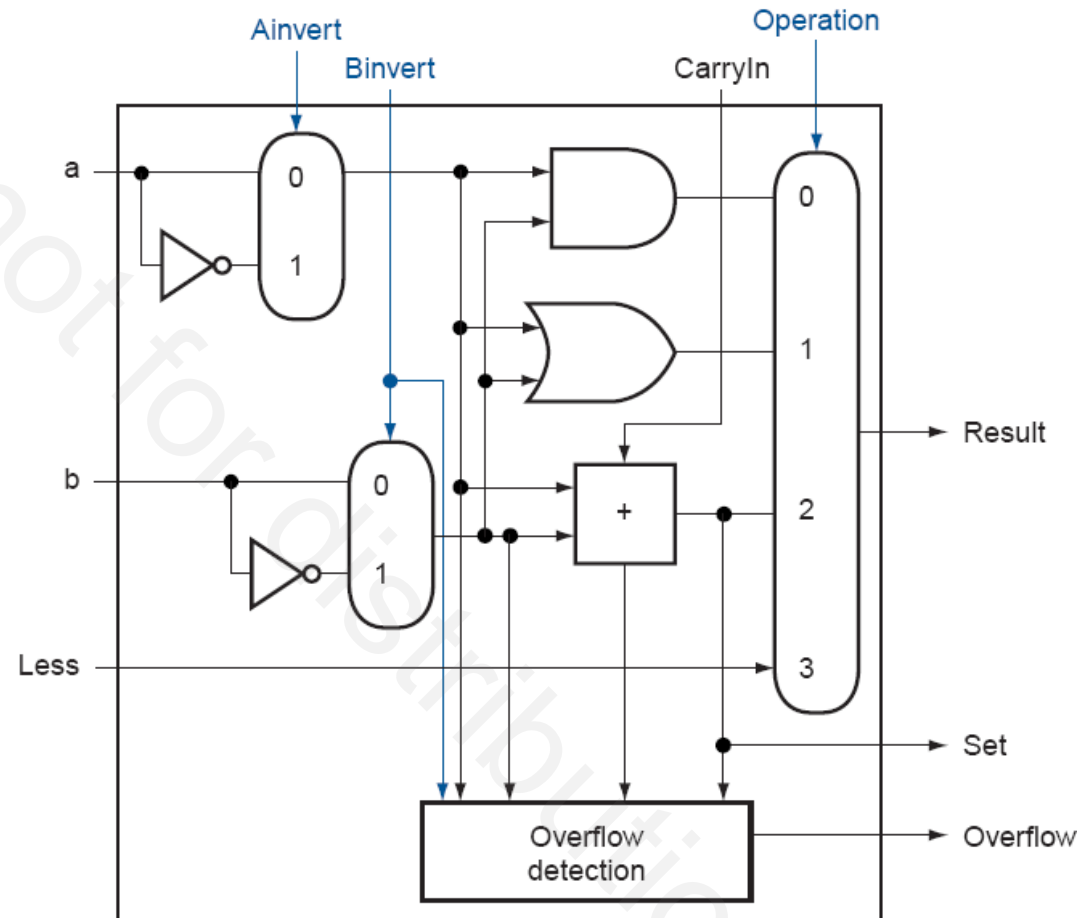


Zero Detection

- Conditional branch instructions check if two registers are equal or unequal
 - do subtraction and see if the result is 0
- Needs simple hardware for NOR-ing 32 output bits:

$$Zero = \overline{(result31 + result30 + \dots + result2 + result1 + result0)}$$

32-bit MIPS ALU

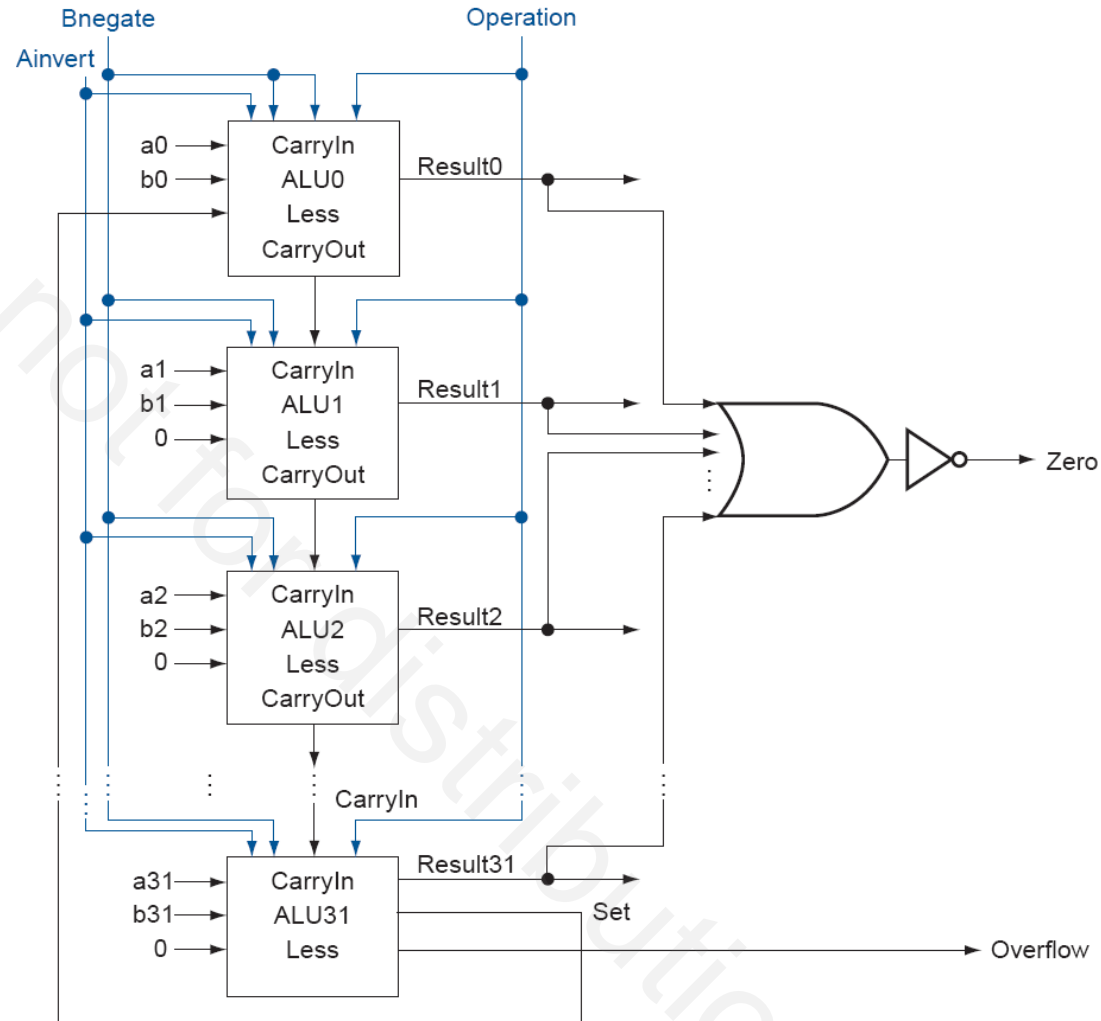
- 4-bit control signals:
 - 2-bits for **Operation**
 - 1-bit for **B_{negate}** line
 - 1-bit for **A_{invert}** line



Gate Count


- How many gates are required by

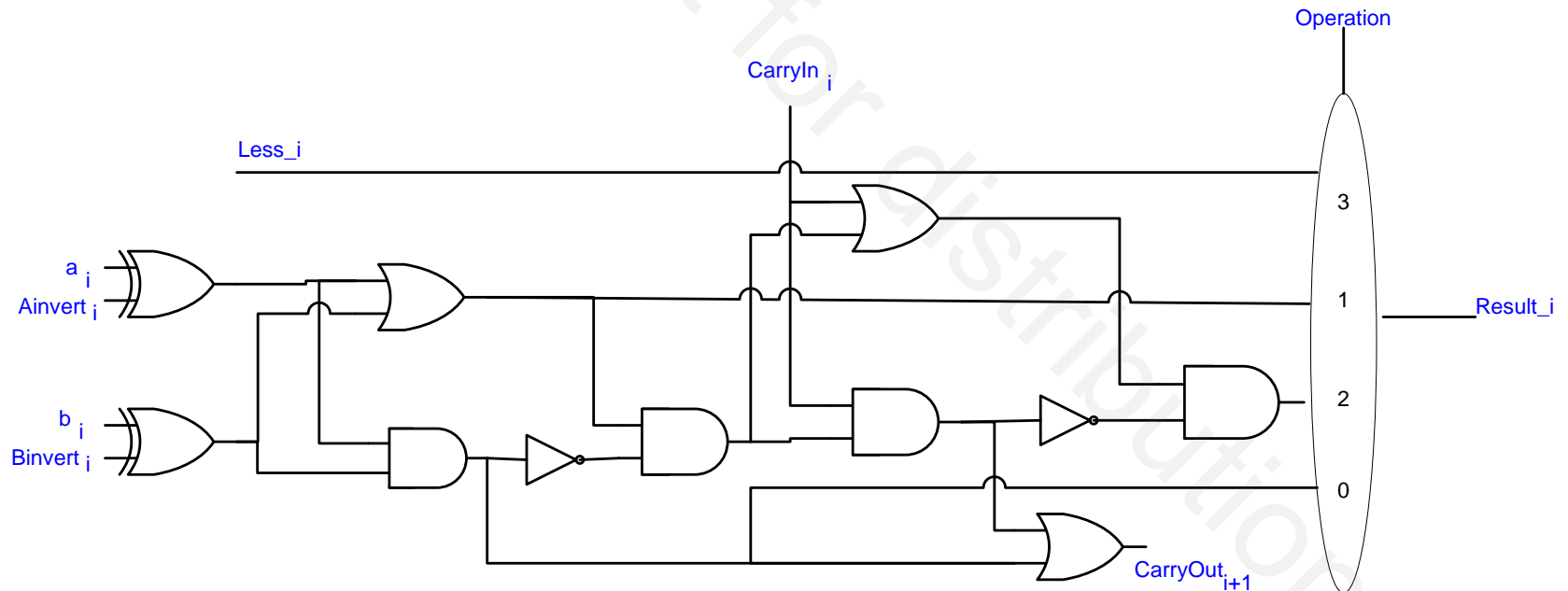- 1-bit ALU?
- 32-bit ALU?
- n-bit ALU?
- Assume AND/OR = 1gate, MUX=5gates, XOR=3gates, Inv=1gate



Gate Delays

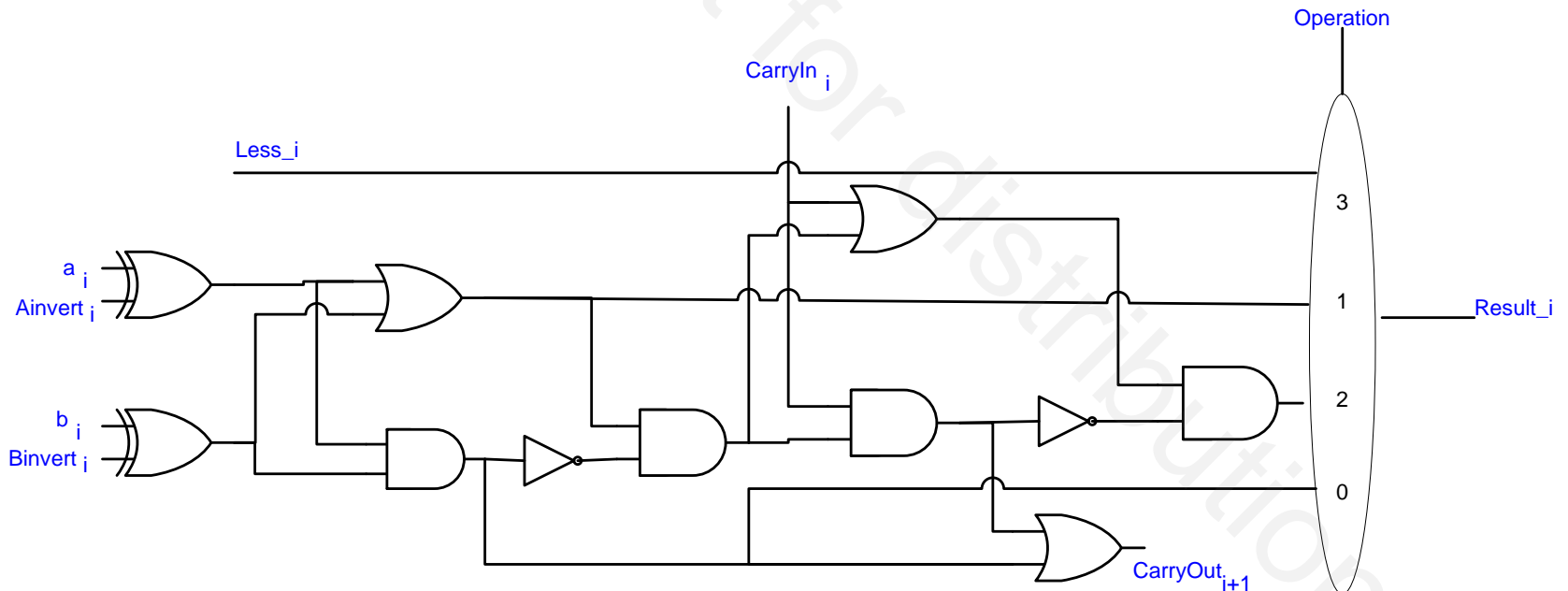- What is the delay of
 - 1-bit ALU?
 - 32-bit ALU?
 - n-bit ALU?
- Assume delays for AND/OR = $1t$, MUX = $2t$, XOR = $2t$, Inv = $1t$



Faster Addition

- The key to speeding up addition is determining the carry into the higher order bits sooner
- With Carry Lookahead Adder (CLA), carries are computed in parallel

Summary

- An n -bit ALU can be designed by cascading n 1-bit ALUs
- ALU functionality is increased by adding more control signals and inputs to multiplexors
- Carry lookahead adders are used for fast addition
- Different design options are available for ALU implementations
 - Decision based on area, power and speed requirements